

# Button Matrix - Documentation

## 1 Circuit Board

### 1.1 Schematic

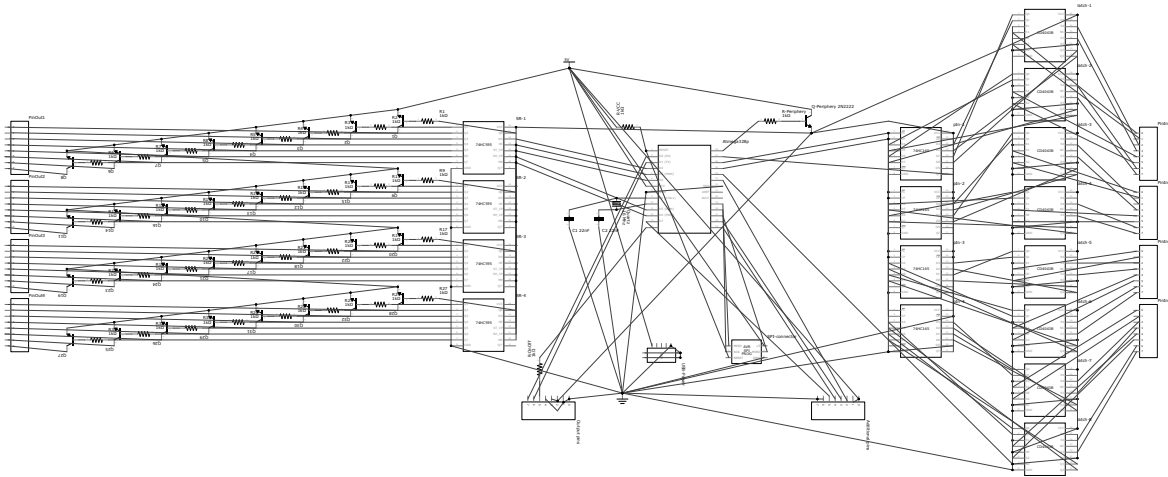


Figure 1: Schematic view of the circuit board design.

### 1.2 Layout - Top

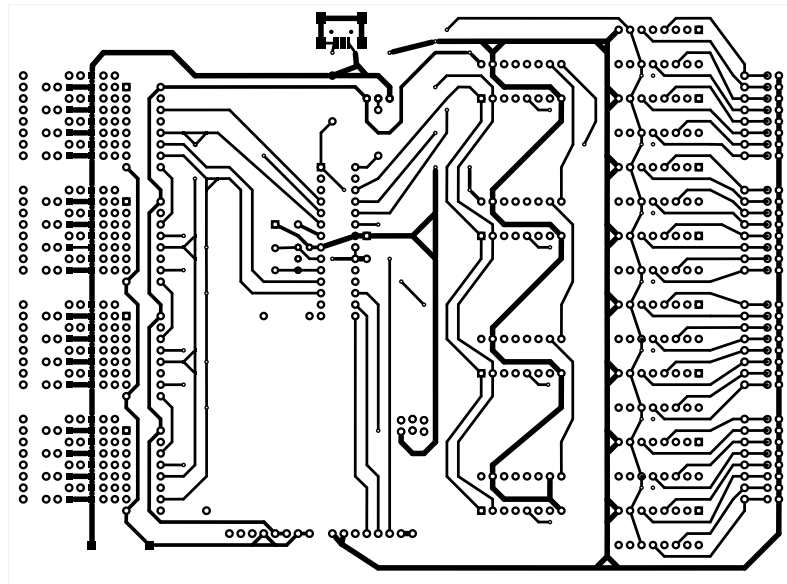


Figure 2: View of the circuit board top as seen from the top.

### 1.3 Layout - Bottom

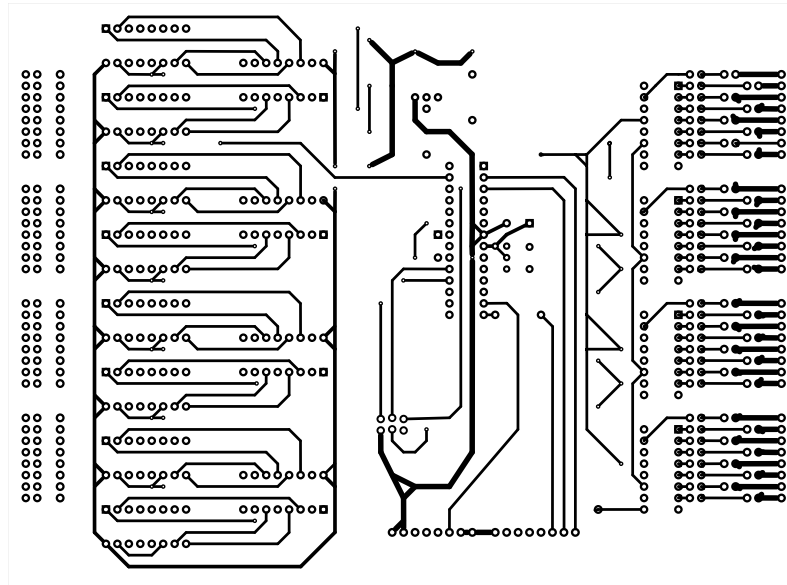


Figure 3: View of the circuit board bottom as seen from the bottom.

### 1.4 Layout - Hardware

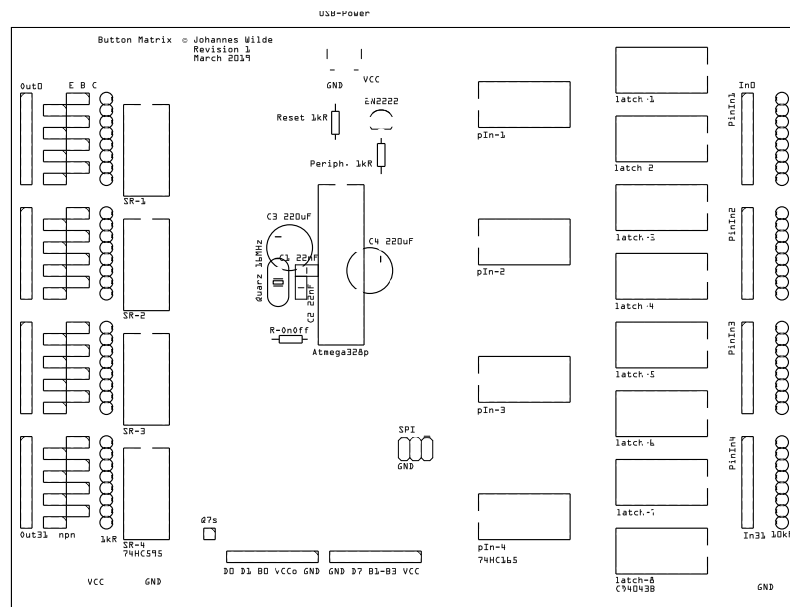


Figure 4: Positioning of the hardware as seen from the top.

## 2 Hardware Description

### 2.1 74HC595 - 8-bit Shift Register

 


Figure 5: Schematic of the 8-bit shift register 74HC595.

Working principle:

The shiftregister has an internal  $[q_i, i \in [0, 7]]$  and an external  $[Q_i, i \in [0, 7]]$  8-bit register. On a rising edge on SRCLK the values  $q_i$  are shifted to  $q_{i+1}$  [ $i \in [0, 6]$ , higher  $i$  first] and SER to  $q_0$ .

On a rising edge on RCLK the values of  $q_i$  are copied to  $Q_i$  [ $i \in [0, 7]$ ]. These will only be visible externally if  $\overline{OE}$  is LOW [otherwise the outputs will be in a high impedance state].

A LOW on  $\overline{SRCLR}$  will set  $q_i$  [ $i \in [0, 7]$ ] LOW.

VCC and GND are required for the shift-register to work.

$q_7$  can be used to pass the out-shifted bits on to another shift-register, if  $q_7$  is connected to SER of the next shift-register [which will have to be clocked accordingly].

$Q_i$  - Output  $i$ ; GND - Ground;  $q_7$  - Serial output;  $\overline{SRCLR}$  - Clear internal shift-register on LOW; RCLK - Copy internal to external shift-register; SRCLK - shift in SER on rising edge;  $\overline{OE}$  - Output Enable; SER - Serial input; VCC - Supply Voltage.

### 2.2 74HC165 - 8-bit parallel in, serial out register

 


Figure 6: Schematic of the parallel in, serial out IC 74HC165.

Working principle:

The parallel load, serial out IC has an internal  $[d_i, i \in [0, 7]]$  and an external  $[D_i, i \in [0, 7]]$  8-bit register.

When  $\overline{PL}$  is LOW the  $D_i$  are copied to the  $d_i$  [ $i \in [0, 7]$ ] asynchronously, i.e. without the need

for a clock.

When  $\overline{PL}$  is HIGH the 74HC165 will function as a shift-register: on a positive edge on CP [if  $\overline{CE}$  is low] the values  $d_i$  are shifted to  $d_{i+1}$  [ $i \in [0, 6]$ , higher  $i$  first] and SER to  $d_0$ . Additionally the complementary signal of the new  $d_7$  will be visible on  $\overline{d_7}$ .

VCC and GND are required for the 74HC165 to work.

$d_7$  can be used to pass the out-shifted bits on to another 74HC165, if  $d_7$  is connected to SER of the next 74HC165 [which will need to have  $\overline{PL}$  low,  $\overline{CE}$  low and be clocked accordingly].

$\overline{PL}$  - Not Parallel Load; CP - Clock;  $D_i$  - Parallel Data In;  $d_7$  - Serial Output;  $\overline{d_7}$  - Not Serial Output; GND - Ground; SER - Serial In;  $\overline{CE}$  - Not Clock Enable; VCC - Supply Voltage.

## 2.3 CD4043B - CMOS Quad 3-State R/S-Latches [NOR]

 


Figure 7: Schematic of the quad 3-state R/S Latch CD4043B.

Table 1: Functional states of the quad 3-state R/S Latch CD4043B [ $i \in [0, 3]$ ].

$S_i$	$R_i$	OE	$Q_i$
X	X	LOW	high impedance
LOW	LOW	HIGH	unchanged
HIGH	LOW	HIGH	HIGH
LOW	HIGH	HIGH	LOW
HIGH	HIGH	HIGH	HIGH

Working principle:

OE controls whether the outputs  $Q_i$  [ $i \in [0, 3]$ ] are connected [OE is HIGH] or in a high-impedance state [like an open circuit; OE is LOW].

Each separate output  $Q_i$  [ $i \in [0, 3]$ ] can be set to HIGH [ $S_i$  HIGH] or reset to LOW [ $R_i$  HIGH] separately and asynchronously.

In case  $S_i$  and  $R_i$  are HIGH simultaneously, the respective output  $Q_i$  will read HIGH.

NC is not connected internally.

$Q_i$  - Output  $i$ ;  $R_i$  - Reset  $i$ ;  $S_i$  - Set  $i$ ; OE - Output Enable; GND - Ground; NC - Not Connected; VCC - Supply Voltage.

 


Figure 8: Schematic view of a LED and its representation in circuit diagrams.

 


Figure 9: Schematic top view onto a npn-transistor and its representation in circuit diagrams.

## 2.4 LED

## 2.5 npn-Transistor

## 2.6 Periphery